

1. Code Debugging and Simulation (10pts)

- 3 A. (6pts) Identify syntax and semantic errors. Correct them and put annotations.
Miss one error or mistake one error will minus 1 point until 0.

```

module value_multiplier
    clk, // Clock
    rst_n, // Asynchronous reset active low
    valueA,
    valueB,
    valueSum,
    ;
input clk;
input rst_n;
input [3:0] valueA;
input [3:0] valueB;
output [7:0] valueSum;

reg [3:0] valueA_r, valueB_r;
reg [7:0] valueSum_r;
reg [7:0] valueA_sgnExt, valueB_sgnExt;
reg [7:0] multiply_result;

assign valueA_sgnExt = {4{valueA_r[3]}, valueA_r};
assign valueB_sgnExt = {4{valueB_r[3]}, valueB_r};
assign multiply_result = valueA_sgnExt * valueB_sgnExt;
assign valueSum = valueSum_r;
    
```

Handwritten annotations and corrections:

- Module Name:** `value_multiplier` (circled 1). Note: "special character 删除, 把 ② 令其改成 value_multiplier".
- Semicolon:** A semicolon at the end of the module definition is circled (2). Note: "多一个分号, 不用加" and "少一个分号, ③".
- Register Declaration:** `reg [7:0] valueA_sgnExt, valueB_sgnExt;` is circled (5). Note: "signed extension 1; {}" and "⑤".
- Register Declaration:** `reg [7:0] multiply_result;` is circled (4). Note: "应改成 wire [7:0]" and "④".
- Assign Statement:** `assign valueA_sgnExt = {4{valueA_r[3]}, valueA_r};` has `valueA_r` underlined.
- Assign Statement:** `assign valueB_sgnExt = {4{valueB_r[3]}, valueB_r};` has `valueB_r` underlined.
- Assign Statement:** `assign multiply_result = valueA_sgnExt * valueB_sgnExt;` is correct.
- Assign Statement:** `assign valueSum = valueSum_r;` is correct.

```

always (posedge clk or negedge rst_n) begin
    if (rst_n !rst_n) begin
        valueA_r <= 0;
        valueB_r <= 0;
        valueSum_r <= 0;
    end else begin
        valueA_r <= valueA;
        valueB_r <= valueB;
        valueSum_r <= multiply_result;
    end
end
endmodule

```

Handwritten notes:
 - $(!rst_n)$
 - negedge reset 要用 !rst_n 或 $\neg rst_n$
 - (b)


Handwritten binary addition:

```

  1 1 1 0 1 0 0 0
+ 0 0 0 1 0 1 0 0
-----
 64 32 16 8 4 2 1 0
 0 0 1 1 0 0 0 0
 1 1 0 0 1 1 1 1
 1 1 0 1 0 0 0 0
 0 0 1 0 1 0 0 0
-----
 1 1 0 1 0 1 1 1

```

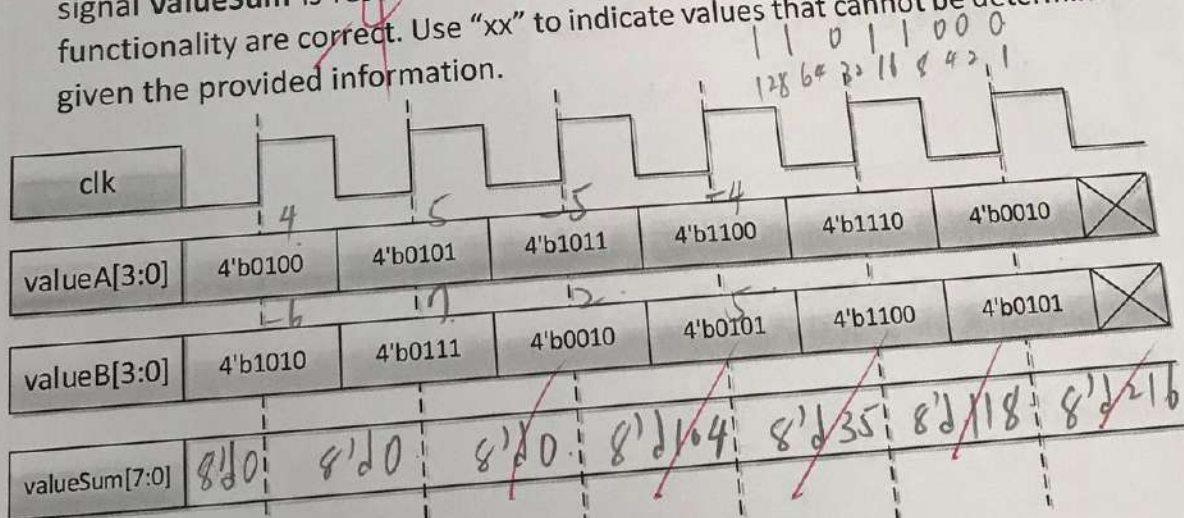B. (4pts) Please show the waveform for the circuit in part A. Suppose that the signal **valueSum** is reset to zero in the beginning and all the syntax error and functionality are correct. Use "xx" to indicate values that cannot be determined given the provided information.



Handwritten values for the signals:

Signal	Cycle 1	Cycle 2	Cycle 3	Cycle 4	Cycle 5	Cycle 6	Cycle 7
valueA	0	4	5	-5	-4		
valueB	0	-6	7	2	5		
mul. sum	0	-24	35	-10	-20		

2. Finite State Machine and Simulation (8pts)

Given a Finite-State-Machine (FSM) as below.

```
module FSM (clk, rst_n, in, out_r);
    parameter S0 = 2'b00, S1 = 2'b01, S2 = 2'b10, S3 = 2'b11;

    input clk, rst_n, in;
    output [1:0] out_r;

    reg [1:0] out_r, out;
    reg [1:0] state_c, state_n;



    always @(*) begin
        case(state_c)
            S0: state_n = (in == 1'b0) ? S2 : S0;
            S1: state_n = (in == 1'b0) ? S0 : S3;
            S2: state_n = (in == 1'b1) ? S1 : S3;
            S3: state_n = (in == 1'b1) ? S2 : S1;
        endcase
    end

    always @(posedge clk or negedge rst_n) begin
        if(~rst_n) begin
            state_c <= S0;
            out_r <= 2'b00;
        end
        else begin
            state_c <= state_n;
            out_r <= out;
        end
    end

    always @(*) begin
        out[1] = in ^ state_c[1];
        out[0] = in & state_c[0];
    end
endmodule
```

(a) (3pts) Please draw a Mealy state transition graph below for this FSM.

Example

  

- (b) (5pts) The FSM is included as a design under test (DUT) in the testbench. After simulation, the terminal shows the outputs. Please design a DUT and input pattern to test all the possible paths (include self-loops) based on operations of the FSM within the given period.

(You should only change the value of **in** on **negedge clk**)

```
module testbench;
reg clk, rst_n, in;
wire [1:0] out_r;
FSM DUT(.clk(clk), .rst_n(rst_n), .in(in), .out_r(out_r));
always @(*) begin
    $monitor("%t clk=%b rst_n=%b in=%b state_c=%d out_r=%b",
            $time, clk, rst_n, in, DUT.state_c, out_r);end
// ...
endmodule
```

Monitor Output Response:

Time	clk	rst_n	in	state_c	out_r
0	1	0	1	S0	00
1	0	1	1	S0	00
2	1	1	1	S0	10
3	0	1	0	S0	00
4	1	1	0	S2	10
5	0	1	0	S2	10
6	1	1	0	S3	10
7	0	1	1	S3	01
8	1	1	1	S2	00
9	0	1	1	S2	00
10	1	1	1	S1	11
11	0	1	1	S1	11
12	1	1	1	S3	01
13	0	1	0	S3	10
14	1	1	0	S1	00
15	0	1	0	S1	00
16	1	1	0	S0	00

00

3. Logic Synthesis + Blocking & Non-Blocking (12 pts)


Please draw the corresponding circuits (in the right column) according to the Verilog codes (in the left column). You can use AND, OR, NAND, NOR, XOR, XNOR, NOT, MUX, D Flip-Flop, Latch, Shifter, Adder, Multiplier in the circuit diagram.

<p>(a) Verilog Code (3 pts)</p> <pre> always @(*) begin X = A + B << 2; Z = C D; Y = (~Z) ? X : Q; end </pre>	<p>Circuit Diagram</p>
<p>(b) Verilog Code (3 pts)</p> <pre> always @(posedge clk) begin A <= D; B <= A ~^ D; C <= ~B; D <= C ^ D; end </pre>	<p>Circuit Diagram</p>
<p>(c) Verilog Code (3pts)</p> <pre> always @(A or B or C) begin if (~C) D = A & B; end </pre>	<p>Circuit Diagram</p>
<p>(d) Verilog Code (3pts)</p> <pre> always @(posedge clk) begin if (C) D <= A ~B; end </pre>	<p>Circuit Diagram</p>

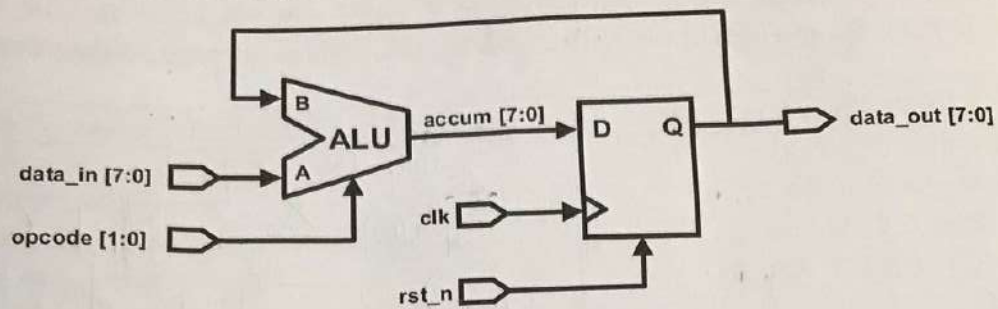4. Verilog Design (6pts)

+55

A design with an ALU unit and its description of functions are shown below.



Signal	Description
clk	Input clock
rst_n	Input asynchronous negative reset
data_in [7:0]	Input unsigned data
accum [7:0]	Result from ALU
data_out [7:0]	Output unsigned data (positive clock edge triggered)
opcode [1:0]	Input operation control signals

opcode	ALU operation
2'b00	A + B
2'b01	A - B
2'b10	A XOR B
2'b11	A NOR B

(6pts) Please complete the Verilog code of this counter (you **don't** have to consider overflow in this design).

```
module alu_design (clk, rst_n, opcode, data_in, data_out);
```

I/O & Reg/Wire Declaration (1pt)

```
input clk, rst_n;
input [1:0] opcode;
input [7:0] data_in;
output [7:0] data_out;
```

// You can declare new signals here if you need

```
reg [7:0] accum;
assign data_out = accum;
```


Combinational Logic for the Counter (3pts)

```
always @ (*) begin
```

```
    case (opcode)
        2'b00: accum_h = data_in + data_out;
        2'b01: accum_h = data_in - data_out;
        2'b10: accum_h = data_in ^ data_out;
        2'b11: accum_h = data_in & data_out;
    endcase
```

```
end
```

Sequential Logic for the Counter (2pts)

```
always @ (posedge clk or negedge rst_n) begin
```

```
    if (~rst_n) begin
        accum <= 8'd0;
```

```
    end else begin
        accum <= accum_h;
```

```
end
```

```
endmodule
```

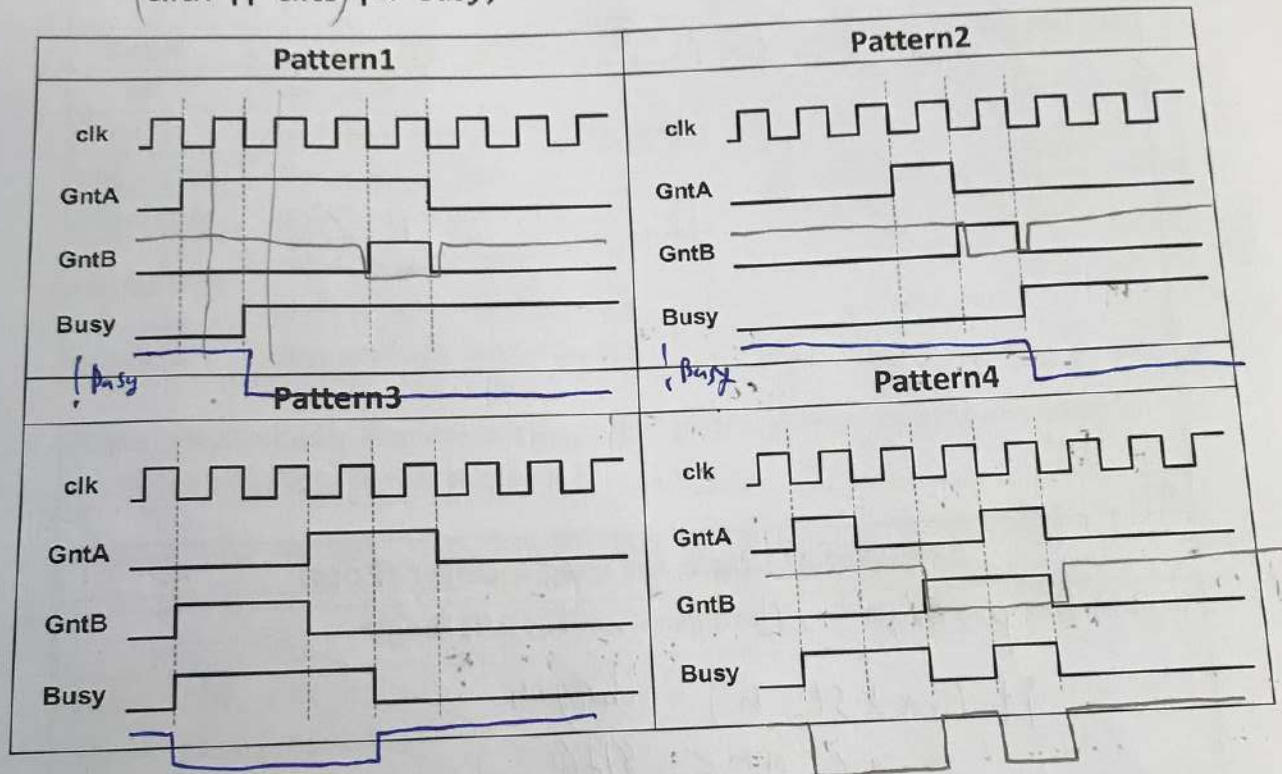

5. Formal Verification (9pts)

Consider 3 assertions and 4 patterns below. Please identify the patterns which are violated for each assertion.

(a) assert_0: assert property (@(posedge clk)
!(GntB && !Busy))

(b) assert_1: assert property (@(posedge clk)
GntA && !GntB |> ##[0:2] Busy)

(c) assert_2: assert property (@(posedge clk)
(GntA || GntB) |> Busy)




(9 pts) Fill in Pass/Fail in each block.

	Pattern1	Pattern2	Pattern3	Pattern4
(a)	Pass	Fail	Pass	Fail
(b)	Fail	Pass	Fail	Fail
(c)	Pass	Fail	Fail	Fail

10/21

 6. Timing path & Setup/hold time (22pts)

Consider the circuit and the delay information below. Answer the following questions.



Operation	\oplus	\otimes	$ \cdot $	x^2
Min Delay (ns)	0.5	3.0	0.2	1.5
Max Delay (ns)	1.0	4.0	0.5	2.0

A. (5pts) List all timing paths. How many timing paths in total? (e.g. A \rightarrow S1/D)

共 3 case

1. A \rightarrow S2/D : $t_{pd} = 4$
 $t_{cd} = 3$

2. B \rightarrow S1/D : $t_{pd} = 0$
 $t_{cd} = 0$

3. S1/clock \rightarrow S2/D : $t_{pd} = 2 + 4 = 6$
 $t_{cd} = 2 \cdot 0.5 + 3 = 4$

4. S1/clock \rightarrow S3/D : $t_{pd} = 1$
 $t_{cd} = 0.5$

5. S2/clock \rightarrow C : $t_{pd} = 2$
 $t_{cd} = 1.5$

6. S2/clock \rightarrow S2/D : $t_{pd} = 2 + 4 + 1 = 7$
 $t_{cd} = 0.5 + 1.5 + 3 = 5$


7. S3/clock \rightarrow S2/D : $t_{pd} = 0.5 + 2 \times 1 + 4 = 6.5$
 $t_{cd} = 0.2 + 2 \times 0.5 + 3 = 4.2$

8. S3/clock \rightarrow S3/D : $t_{pd} = 1.5$
 $t_{cd} = 0.7$

8 in total

11/21

B. Setup/Hold time constraint

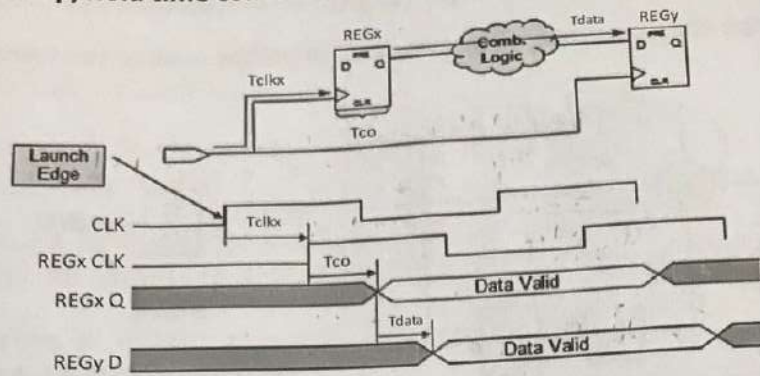

Following the circuit in 6.A. The registers' timing diagrams are shown above. $T_{co} = 0.5ns$, and $T_{clk} = 0.3ns$ are the same for every register. Assuming that T_{setup} (Setup Time) = $0.4ns$, T_{hold} (Hold Time) = $0.1ns$, and $D_A = D_B = D_C = 1.5ns$. The circuit operates at the clock frequency of **125MHz**.

B1. (5pts) Check that whether there are setup time violations or not by showing if the related inequalities for all timing paths are satisfied. If setup time violation(s) occur, identify the violated path(s). $\rightarrow T_{data} = T_{pd}$.

125 MHz $\rightarrow T_{period} = \frac{1}{125 \times 10^6} = 8ns$

① $Sx/dk \rightarrow Sx/D$ $T_{clkx} + T_{co} + T_{data} + T_{su} \leq T_{period} + T_{clkx}$
 $T_{su} \leq T_{period} - T_{clkx} - T_{co} - T_{data} + T_{clkx}$

② $A, B \rightarrow Sx/D$ $D_A + T_{data} + T_{su} \leq T_{period} + T_{clkx}$ $\rightarrow T_{su} \leq T_{period} - D_A - T_{data} + T_{clkx}$
 $D_C + T_{su} \leq T_{period}$ $\rightarrow T_{su} \leq T_{period} - D_C$

③ $Sx/D \rightarrow C$ $D_C + T_{su} \leq T_{period}$ $\rightarrow T_{su} \leq T_{period} - D_C$

1, $T_{su} \leq 8 + 0.3 - 1.5 - 4 = 3.8 (V)$ ✓
 2, $T_{su} \leq 8 + 0.3 - 1.5 = 6.8 (V)$ ✓
 3, $T_{su} \leq 8 - 0.5 - 6 = 1.5 (V)$ ✓
 4, $T_{su} \leq 8 - 0.5 - 1 = 6.5 (V)$ ✓
 5, $T_{su} \leq 8 - 0.5 - 2 = 5.5 (V)$ ✓
 6, $T_{su} \leq 8 - 0.5 - 1 = 6.5 (V)$ ✓
 7, $T_{su} \leq 8 - 0.5 - 6.5 = 1 (V)$ ✓
 8, $T_{su} \leq 8 - 0.5 - 1.5 = 6 (V)$ ✓

\Rightarrow all path pass

12/21

B2. (5pts) Check that whether there are hold time violations or not by showing if the related inequalities for all timing paths are satisfied. If hold time violation(s) occur, identify the violated path(s). $\Rightarrow T_{cd} = T_{data}$ from A.1

cases
1, 2, 3, 4

$$(Sx/clk + Sx/D) T_{clk} + T_{cot} + T_{dora} \geq T_{hold} + T_{clkx}$$

$$\Rightarrow T_{hold} \leq T_{cot} + T_{dora} + T_{clkx} - T_{clkx}$$

$$(2) A, B \rightarrow Sx/D_{data} + D_{data} \geq T_{hold} + T_{clk}$$

$$\Rightarrow T_{hold} \leq D_{data} + T_{dora} - T_{clkx}$$

$$(3) Sx/D \rightarrow C \rightarrow D_{data} \geq D_{data} \geq T_{hold} + 0$$

1	$T_{hold} \leq 1,5 + 3 - 0,3 = 4,2$ (V)	5	$T_{hold} \leq 1,5$ (V) X
2	$T_{hold} \leq 1,5 + 0 - 0,3 = 1,2$ (V)	6	$T_{hold} \leq 0,5 + 5 = 5,5$ (V)
3	$T_{hold} \leq 0,5 + 4 = 4,5$ (V)	7	$T_{hold} \leq 0,5 + 4,2 = 4,7$ (V)
4	$T_{hold} \leq 0,5 + 0,5 = 1$ (V)	8	$T_{hold} \leq 0,5 + 0,7 = 1,2$ (V)

all path pass

B3. (7pts) Assuming that there is time skew between T_{clk3} and other T_{clk} , the relationship between those parameters is: $T_{clk3} = T_{clk1} + 0,1 * \text{Clk_cycle}$, where $i = 1, 2$. T_{clk1} , T_{clk2} , and other conditions are the same as A2. Explain if there are timing violations in this circuit. If yes, identify the violated path(s).

$$T_{clk3} = T_{clk1} + 0,1 * 8 = 1,1$$

clock period

① set up: find clock skew $\frac{1}{8} \approx 0,125$ path ①

$$T_{su} \leq 8 - 0,5 - 6,5 - 1,1 + 0,3 = 0,2$$

$$0,4 = T_{su} \leq 0,2 \quad \text{path 1} \quad \text{violation}$$

$$(S3/clk + S3/D)$$

② hold time: find clock skew $\frac{1}{8} \approx 0,125$ path ④ Q.E.D.

$$T_{hold} \leq 0,5 + 0,5 + 0,3 - 1,1 = 0,2$$


$$0,1 = T_{hold} \leq 0,2 \quad \text{path 4 pass}$$

① = hold?

② = setup?

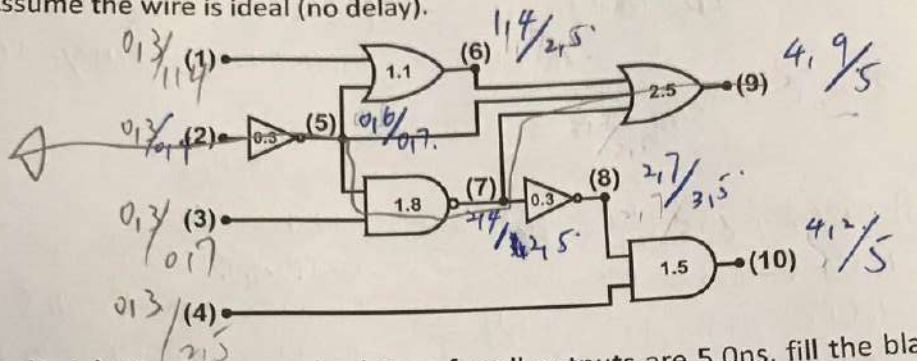7. Slack graph (8pts)

The figure below shows a combinational circuit with primary inputs. The delay of each input is 0.3ns and the delay of every gate is given on the gate (unit: ns). Assume the wire is ideal (no delay).




C1. (5pts) Given the required time for all outputs are 5.0ns, fill the blanks on the form with corresponding arrival time, required time, and slack of every node.

AT = Arrival Time, RT = Required Time.

Node	(1)	(2)	(3)	(4)	(5)
AT (ns)	0.3	0.3	0.3	0.3	0.6
RT (ns)	1.14	0.4	0.7	2.5	0.7
Slack (ns)	1.1	0.1	0.4	2.2	0.1
Node	(6)	(7)	(8)	(9)	(10)
AT (ns)	1.17	2.4	2.7	4.9	4.2
RT (ns)	2.5	2.5	3.5	5	5
Slack (ns)	0.8	0.1	0.8	0.1	0.8

 
C2. (3pts) Please indicate the critical path and show its slack values.



14/21


8. Synthesis (33pts)

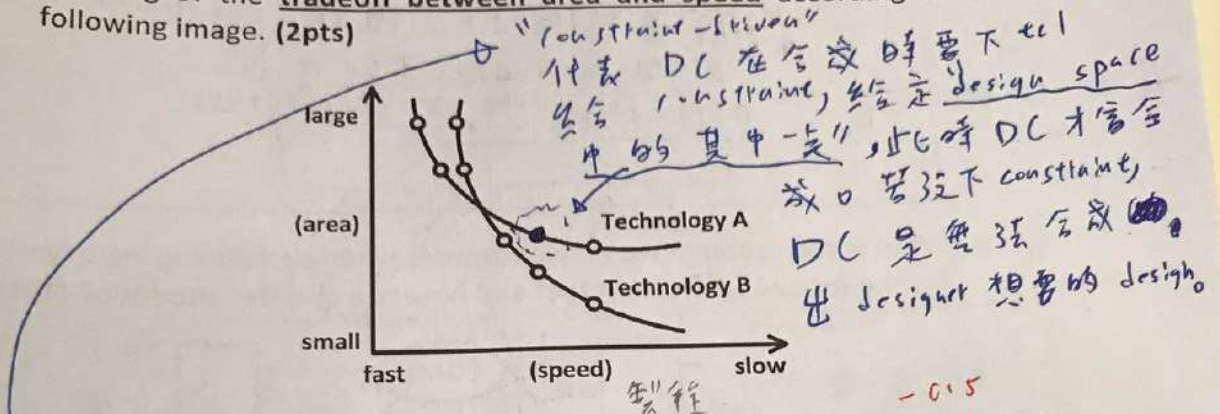1. Please explain why synthesis is constraint-driven and what is the meaning of the tradeoff between area and speed according to the following image. (2pts)



從上圖可以看出不論 A, B, speed 和 area 都成“反比”。負相關
因此, 當我想要 area 小 \Rightarrow design, speed 自然會慢
反之亦然。

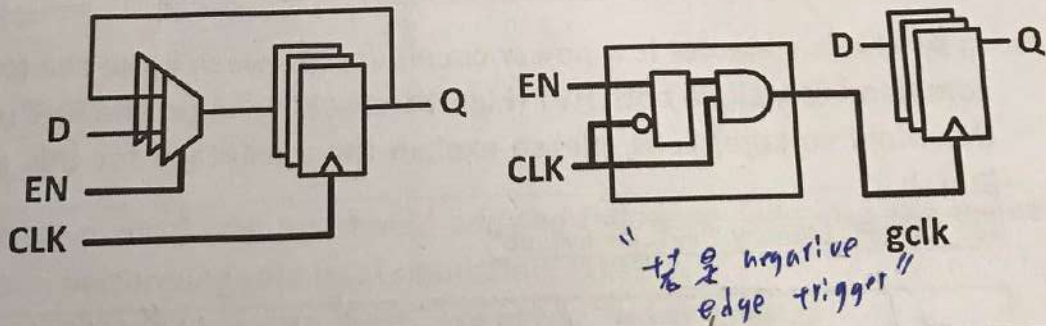2. Why we preferred the architecture on the right hand side instead of left hand side design in clock gating? (2pt)




左邊的 skt 在 clock gating 時會有 glitch, 如下圖 gclk. 因此要用右邊的 Latch 這避免 glitch 生成。gclk.

3. Please explain why should we consider PVT condition when synthesis (1pt) and what does PVT stand for? (1pt)

在 technology library (.db) 中有 PVT conditions, 要用, 要指定此一條件 constraint driven synthesis tool, 才能合成.
process, voltage, temperature.

 4. What is the problem we may encounter when performing logic synthesis for the following circuit? (1pt) and how to avoid this situation? (1pt)



①, STA 分析, timing 不收收敛.


② 打斷 comb loop, 在中間插入一級 register (如图)

5. In synthesis stage for low power circuit design, we will use the following command to include both HVT (high-threshold voltage) and RVT (regular-threshold voltage) cells, please explain the advantage for this process. (2pts)

set_target_library "rvt.db hvt.db"

在 non-critical path 上用 "hvt.db", 使得 threshold voltage 上升, 减少静态放电电流
在 critical path 上用 "rvt.db", 使得 design 有更好的 timing.

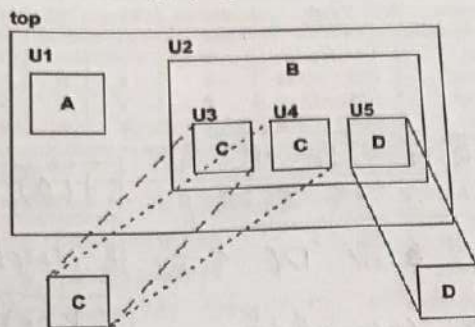6. In a hierarchical design, submodules are sometimes referenced by more than one cell instance. What method is required to solve this situation? (1pt)
And what is the effect after applying this method? (1pt)



- ① 使用 don't touch method, 先合成 submodule, 再合成整個 design。但 submodule 要在底下 don't_touch_command。
- ② compile 速度加快, memory 用量减少, 维持 design Hierarchy.

7. Please explain the difference between RTL Level Netlist and Gate Level Netlist. (1pt)

RTL 沒有 timing 資訊。
但 Gate level 有。

↳ 看不到

8. Please explain why we should add the following code into the testbench when performing gate level simulation. (1pt)

```
$sdf_annotate ("SDF_FILE_NAME", top_module_instance_name);
```

SDF 裡面有 timing 資訊, 若沒有加 SDF file, 則 gate level sim 結果會錯誤, 他會去 TSMC 找 default 的 timing。
造成 sim 結果發生 timing violation,

17/21

9. Why the synthesis report shows register with latch type when loading design? (1pt) and please also explain how to avoid this situation. (1pt)

Register Name	Type	Width	Bus	MB	AR	AS	SR	SS	ST
reg_B_reg	Latch	8	Y	N	Y	N	N	N	N
reg_ins_reg	Flip-flop	4	Y	N	Y	N	N	N	N
alu_out_reg	Flip-flop	8	Y	N	Y	N	N	N	N
reg_A_reg	Flip-flop	8	Y	N	Y	N	N	N	N

RTL code 中

①, max case 3 个 3 个 $y(a) \text{ out} = in;$
 造成 D0 合或出 latch.

② FE case 3 个 3 个 $y(a) \text{ out} = in;$
 else $\text{out} = 0;$

10. Synopsys Design Constraints File (.sdc) specifies the timing constraints for synthesis. Please write the commands might be included in the .sdc file to meet the following specification. (10pts, 1pt for each)

- This design is an ALU with clock port i_clk with 200 MHz operating frequency (1%)
- All flip-flops should meet the hold-time constraints (1%)
- Clock tree synthesis will be built in the place and route stage, so the clock network cannot be re-buffered (1%)
- Clock tree synthesis will be built in the place and route stage, so the clock network is considered with no delay (1%)
- The input delay is considered as $0.1 * \text{clock_cycle}$ (1%)
- The output delay is considered as $0.1 * \text{clock_cycle}$ (1%)
- The operating condition for synthesis should include both slow and fast library for max and min condition (1%)
- The clock latency is considered as $0.05 * \text{clock_cycle}$ (1%)
- The clock transition is considered as $0.01 * \text{clock_cycle}$ (1%)
- The clock skew and jitter are considered as 0.1 ns and 0.2 ns, respectively (1%)

These are only example commands you may use, please choose the correct ones and modify them to meet the abovementioned specification. (you do not have to consider the commands for including library)

- set period 10.0
- set_operating_conditions -max_library slow -max slow
- create_clock -name clk -period 10.0


4. set_dont_touch_network [get_clocks clk]
5. set_ideal_network [get_clocks clk]
6. set_fix_hold [get_clocks clk]
7. set_clock_latency 0.5 [get_clocks clk]
8. set_clock_transition 0.1 [get_clocks clk]
9. set_max_transition 0.1
10. set_input_delay 0.5 -clock clk [all_inputs]
11. set_output_delay 0.5 -clock clk [all_outputs]
12. set_clock_uncertainty 0.1 [get_ports clk]
13. set_load 1 [all_outputs]
14. set_drive 1 [all_inputs]
15. set_false_path -from {A} -through {C} -to {OUT}
16. set_max_delay 1 from [all_inputs] -to [all_outputs]

-0.5
-4
-1

clock
specification

- A, set period 5, create - clock - T - clk - period 5.0
- B, set_fix_hold [get_clocks clk]
- D set_ideal_network [get_clocks clk]
- C. set_dont_touch_network [get_clocks clk]
- E set_input_delay 0.5 -clock clk [all_inputs]
- F set_output_delay 0.5 -clock clk [all_outputs]
- G set_operating_conditions -max_library slow -min_library fast
- H set_clock_latency 0.25 [get_clocks clk]
- I set_clock_transition 0.1 [get_clocks clk]
- J. set_clock_uncertainty 0.1 [get_ports clk]

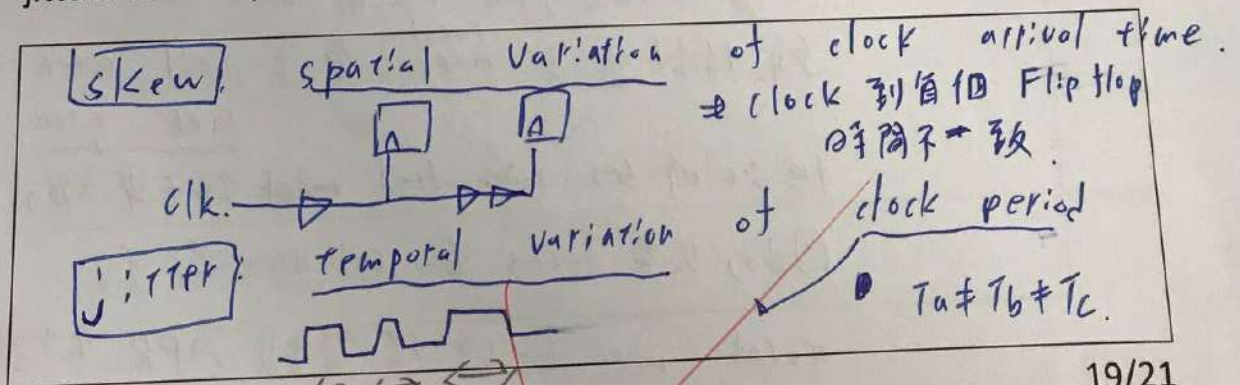11. Two situations are considered for clock uncertainty: clock skew and clock jitter. Please explain the definition of clock skew (1pt) and clock jitter (1pt).



19/21

12. Please read the area synthesis report below and answer the questions:

- How to fix the undefined interconnect area? (1pt)
- If Macro/Black Box area is not zero, what might be indicated? (1pt)
- In cell-based IC design flow, we will mainly focus on total cell area instead of total area, please explain why. (1pt)

```

1 *****
2 Report : area
3 Design : ALU
4 Version: N-2017.09-SP2
5 Date   : Fri Nov 13 12:55:25 2020
6 *****
7
8
9 Library(s) Used:
10 typical (File: /home/raid7_2/course/cvstd/CBDK_IC_Constest/CIC/SynopsysDC/db/typical.db)
11
12
13 Number of ports:      82
14 Number of nets:      204
15 Number of cells:     106
16 Number of combinational cells: 74
17 Number of sequential cells: 30
18 Number of macros/black boxes: 0
19 Number of buf/inv:    10
20 Number of references: 16
21
22 Combinational area:   977.702419
23 Buf/Inv area:         37.342799
24 Noncombinational area: 903.016769
25 Macro/Black Box area: 0.000000
26 Net Interconnect area: undefined
27
28 Total cell area:      1880.719188
29 Total area:           undefined

```

a, see wire load model

b, 使用非 standard cell 之 IP,
例如: HW3 中的 SRAM cell

c, 因为在 DC 时, chip 面积在电路中的
位置不确定, 所以用 wire load model
的估计也 ^{total} 包含 cell area 和
wire area.

但此时的 wire load model 很不准确,
因此, 只需 focus 在 cell area 即可。

total area 之估计等到 APR 验证后

20/21

13. When performing timing analysis with the following command, if there are **only** two paths in the timing report *Design.timing* shown as the following table, please indicate which path is the critical path (1pt) and explain why. (1pt)

report_timing -path full -delay max > Design.timing

Path1			Path2		
Startpoint: V[0] (input port clocked by clk) Endpoint: FB_A[11] (output port clocked by clk) Path Group: clk Path Type: max			Startpoint: V[1] (input port clocked by clk) Endpoint: FB_A[10] (output port clocked by clk) Path Group: clk Path Type: max		
Point	Incr	Path	Point	Incr	Path
clock clk (rise edge)	0.00	0.00	clock clk (rise edge)	0.00	0.00
clock network delay (ideal)	0.50	0.50	clock network delay (ideal)	0.50	0.50
input external delay	5.00	5.50 f	input external delay	5.00	5.50 r
V[0] (in)	0.00	5.50 f	V[1] (in)	0.00	5.50 r
U622/Y (CLKINX1)	0.04	5.54 r	U620/Y (CLKINX1)	0.04	5.55 f
U621/Y (MXI2X1)	0.09	5.63 f	U619/Y (MXI2X1)	0.12	5.66 r
U432/Y (AND2X1)	0.21	5.84 f	U293/CO (ADDFXL)	0.61	6.27 r
U293/CO (ADDFXL)	0.36	6.19 f	U294/CO (ADDFXL)	0.33	6.60 r
U294/CO (ADDFXL)	0.39	6.58 f	U430/Y (AND2X1)	0.19	6.79 r
U430/Y (AND2X1)	0.21	6.79 f	U429/Y (XOR2X1)	0.16	6.95 f
U428/Y (AND2X1)	0.18	6.97 f	U702/Y (MXI2X1)	0.56	7.51 r
U427/Y (XOR2X1)	0.15	7.12 f	U363/Y (INVX12)	0.75	8.26 f
U701/Y (MXI2X1)	0.54	7.66 r	FB_A[10] (out)	0.00	8.26 f
U368/Y (INVX12)	0.74	8.41 f	data arrival time		8.26
FB_A[11] (out)	0.00	8.41 f	clock clk (rise edge)	10.00	10.00
data arrival time		8.41	clock network delay (ideal)	0.50	10.50
clock clk (rise edge)	10.00	10.00	clock uncertainty	-0.10	10.40
clock network delay (ideal)	0.50	10.50	output external delay	-0.50	9.90
clock uncertainty	-0.10	10.40	data required time		9.90
output external delay	-0.50	9.90	data required time		9.90
data required time		9.90	data arrival time		-8.26
data required time		9.90	slack (MET)		1.64
data arrival time		-8.41			
slack (MET)		1.49			

a, "Path 1"

b, 因其 slack 较小, 代表 timing 比 Path 1 要很多
(= required - arrival time)