

Computer-Aided VLSI System Design
Midterm Examination
2019. 11. 21

Name 吳牧庭
Student ID R08943094

Instructions

This is a **CLOSED** book exam. The exam is to be completed in **180** minutes. If you need scratch paper, just use the blank parts of these pages; show all of your work on these pages. Before you start writing, please check if you have all **18** pages of the exam. **Note that your raw score of this exam will be normalized to 100 points.**

Score Board (to be filled by TAs)

	Points	Score		Points	Score
Problem 1	10	6	Problem 6	20	17
Problem 2	10	10	Problem 7	7	6
Problem 3	10	10	Problem 8	35	30+1
Problem 4	10	10			
Problem 5	3	3	Total	105	92+1

1. (10pts) Code Debugging and Simulation

A. (6pts) Identify syntax and semantic errors. Correct them and put annotations.

+6 Miss one error or mistake one error will minus 1 point until 0.

```
1 module 2value multiplier {  
2     clk,    (/Clock //  
3     rst_n,  (/Asynchronous reset active low  
4     valueA,  
5     valueB, //  
6     valueSum  
7 );  
8  
9     input clk;  
10    input rst_n;  
11    input [3:0] valueA;  
12    input [3:0] valueB;  
13  
14    reg [3:0] valueA_r, valueB_r;  
15    reg [7:0] valueSum_r;  
16  
17    reg [7:0] valueA_sgnExt, valueB_sgnExt;  
18  
19    wire [7:0] valueSum;  
20  
21    wire [7:0] multiply_result;  
22  
23    assign valueA_sgnExt = {4{valueA_r[3]}, valueA_r};  
24    assign valueB_sgnExt = {4{valueB_r[3]}, valueB_r};
```

Annotations:

- Line 1: `module 2value multiplier` → `module multiplier` (need to start with a letter)
- Line 2: `(/Clock` → `clock` (cannot contain white space)
- Line 3: `(/Asynchronous reset active low` → `reset` (cannot contain white space)
- Line 4: `valueB, //` → `valueB` (cannot contain white space)
- Line 5: `valueSum` → `valueSum_r` (semantic error: variable not declared)
- Line 6: `);` → `endmodule` (syntax error: semicolon)
- Line 17: `reg [7:0] valueA_sgnExt, valueB_sgnExt;` → `wire [7:0] valueA_sgnExt, valueB_sgnExt;` (semantic error: registers used for signals)
- Line 19: `wire [7:0] valueSum;` → `output [7:0] valueSum;` (semantic error: wire used for output)

```
assign multiply_result = valueA_sgnExt * valueB_sgnExt;
```

```
assign valueSum = valueSum_r;
```

```
always@ (posedge clk or negedge rst_n) begin
```

```
10 if (!rst_n) begin
```

```
valueA_r <= 0;
```

```
valueB_r <= 0;
```

```
11 valueSum_r <= 0; end
```

```
12 else begin
```

```
valueA_r <= valueA;
```


```
valueB_r <= valueB;
```

```
13 valueSum_r <= multiply_result; end
```

```
end
```

```
14 endmodule
```

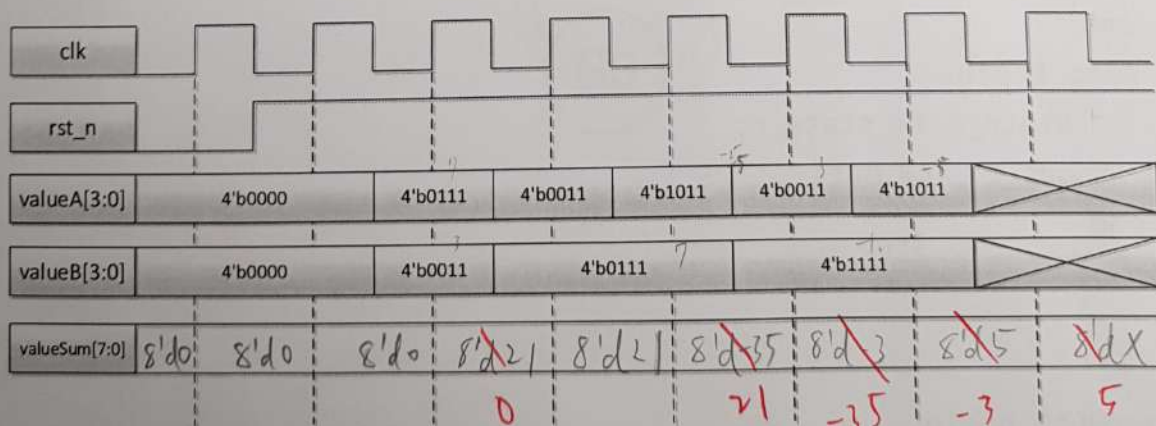B. (4pts) Please draw the waveform for the circuit in part A. You can write value in signed decimal or binary format. Use "xx" to indicate values that cannot be determined given the provided information.



2. Finite State Machine and Simulation (10pts)

Given a Finite-State-Machine (FSM) as below.

```
module FSM (clk, rst_n, in, out_r);
    parameter S0 = 2'b00, S1 = 2'b01, S2 = 2'b10, S3 = 2'b11;

    input  clk, rst_n, in;
    output [1:0] out_r;

    reg [1:0] out_r, out;
    reg [1:0] state_c, state_n;



    always @(*) begin
        case(state_c)
            S0: state_n = (in == 1'b1)? S2 : S0;
            S1: state_n = (in == 1'b1)? S0 : S3;
            S2: state_n = (in == 1'b0)? S1 : S3;
            S3: state_n = (in == 1'b0)? S2 : S1;
            default: state_n = 2'b01;
        endcase
    end

    always@(posedge clk or negedge rst_n) begin
        if(~rst_n) begin
            state_c <= S0;
            out_r    <= 2'b00;
        end
        else begin
            state_c <= state_n;
            out_r    <= out;
        end
    end

    always@(*) begin
        out[1] = in ^ state_c[1];
        out[0] = in ^ state_c[0] ^ state_c[1];
    end
end
```

+5
(a) (5pts) Please draw a state transition graph below for this FSM.

Example

  

- ^{TS}
(b) (5pts) The FSM is included as a design under test (DUT) in the testbench. After simulation, the command window shows the outputs. Please design a DUT (including input pattern) to test all the possible conditions based on operations of the FSM within the given period.

```

module testbench;
reg clk, rst_n;
reg in;
wire [1:0] out_r;
FSM DUT(.clk(clk), .rst_n
(rst_n), .in(in), .out_r(out_r));
always @(*) begin
    $monitor("%t %b %b %b %b %b %b", $time, clk, rst_n, in,
        state_c, state_n, out_r);
end
endmodule

```

Monitor Output Response:

Time	clk	rst_n	in	state_c	state_n	out_r
0	0	1	0	S0	S0	xx
1	1	0	0	S0	S0	00
2	0	1	1	S0	S2	00
3	1	1	1	S2	S3	11
4	0	1	0	S2	S1	11
5	1	1	0	S1	S3	11
6	0	1	1	S1	S3	11
7	1	1	0	S3	S2	01
8	0	1	0	S3	S2	01
9	1	1	0	S2	S1	10
10	0	1	1	S2	S3	10
11	1	1	1	S3	S1	00
12	0	1	1	S3	S1	00
13	1	1	1	S1	S0	01
14	0	1	1	S1	S0	01
15	1	1	0	S0	S0	10
16	0	1	0	S0	S0	10


3. ¹⁰ (10 pts) Logic Synthesis + Blocking & Non-Blocking

Please draw the corresponding circuits (in the right column) according to the Verilog codes (in the left column). You can use AND, OR, NAND, NOR, XOR, XNOR, NOT, MUX, D Flip-Flop, Latch, Shifter, Adder, Multiplier in the circuit diagram.

(a) Verilog Code (2 pts)	Circuit Diagram
<pre> always @(*) begin X = A/4+B*2; Z = C & D; Y = (Z)? X: Q; end </pre>	
(b) Verilog Code (2 pts)	Circuit Diagram
<pre> always @(posedge clk) begin A <= ~D; B <= ~A ^ ~D; C <= ~B; D <= C ^ D; end </pre>	
(c) Verilog Code (3 pts)	Circuit Diagram
<pre> always@(A or B or C) begin if(C) D = ~A & B; end </pre>	
(d) Verilog Code (3 pts)	Circuit Diagram
<pre> always@(posedge clk) begin if (!C) D <= A ~B; end </pre>	

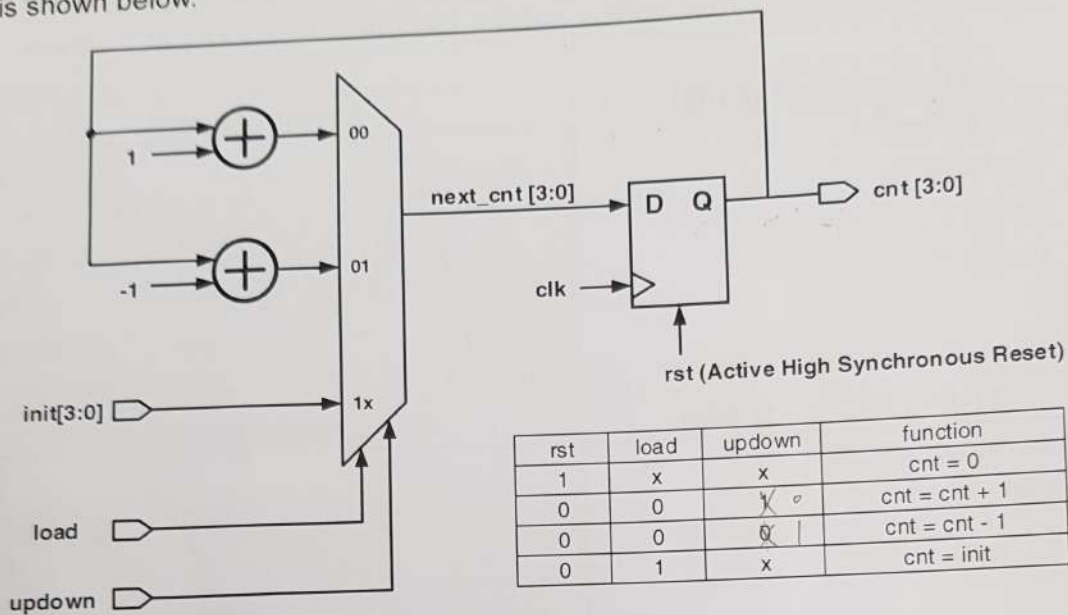4. (10pts) Verilog Design

A counter with synchronized initial value loading and up count/down count function is shown below.



(10pts) Please complete the Verilog code of this counter:

```
module counter (clk, rst, init, load, updown, cnt);
```

I/O & Reg/Wire Declaration

```
input clk, rst;
input [3:0] init;
input load, updown;
```

```
output reg [3:0] cnt;
reg [3:0] next_cnt;
```

// You can declare new signals here if you need

Combinational Logic for the Counter (5pts)

always @ (*) begin

if (load)

next_cnt = init;

else if (updown)

next_cnt = cnt - 1'b1;

else

next_cnt = cnt + 1'b1;

(+10)

end

Sequential Logic for the Counter (5pts)

always @ (posedge clk) begin

if (rst)

cnt ≤ 4'b0;

else

cnt ≤ next_cnt;

end

endmodule

5. (3pts) Operating condition

+3


Fill in High/Low in each block ()

Operational condition	Vt	supply voltage	temperature
fast	low	high	low
slow	high	low	high

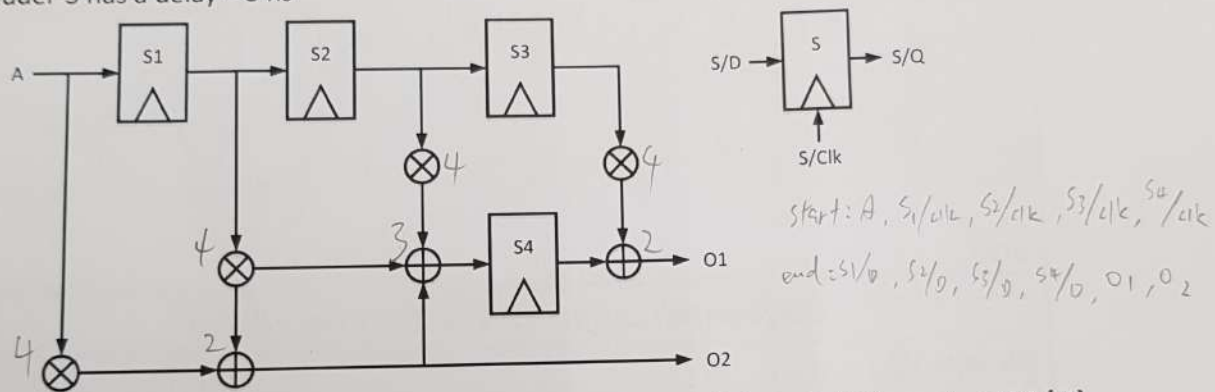6. (20pts) Timing path & Setup/hold time

+17


Consider the circuit below, all multiplier has a delay = 4ns, adder-2 has a delay = 2 ns, adder-3 has a delay = 3 ns



A. (7pts) List all timing path. How much timing path in total? (e.g. A -> S4/D)

A → S1/D, S1/clk → S2/D, S2/clk → S3/D, S3/clk → O1, 10 paths
A → S4/D, S1/clk → S4/D, S2/clk → S4/D, S4/clk → O1
A → O2, S1/clk → O2

B. (13pts) Setup/Hold time constraint

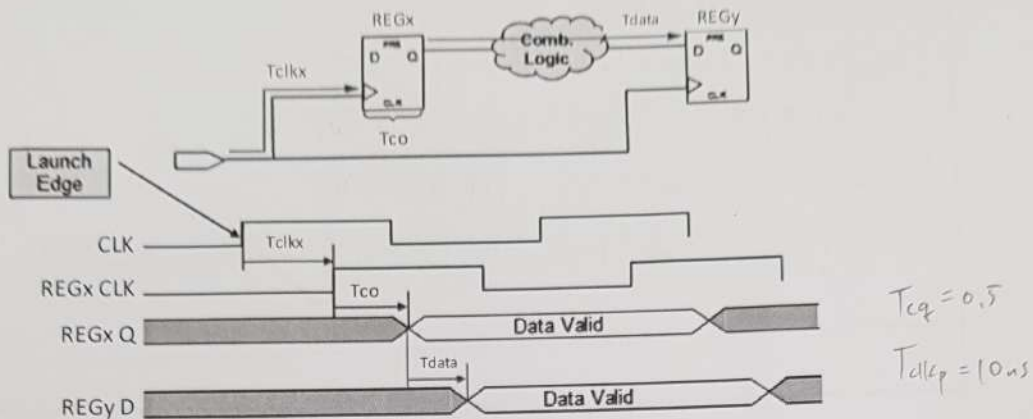

Following the circuit in 5.A. The registers' timing diagrams are shown above, and $T_{co} = 0.5ns$ is same for every register. For register Si, its Tclk is denoted as Tclk_i. The circuit in 5.A. operates at the clock frequency of 100MHz. Suppose that the rise, fall delays for each combinational element are the same, and the input delay of A is D_A , output delay of O1 and O2 are D_{O1} and D_{O2} .

B1. (3pts) Write the timing inequality for setup time in terms of Tclk1, Tclk2, Tclk3, Tclk4, D_A , D_{O1} , D_{O2} .

Handwritten notes on the right side of the diagram:

- $T_{setup} = 0.5$
- $T_{i/o} = 0.5$
- $T_{clk1} = 0.3$
- $T_{clk2} = 0.15$
- slack:

Handwritten setup check:

$$10ns - T_{setup} + T_{clk4} > D_A + 4 + 2 + 3 \quad (A \rightarrow S4/O)$$

$$10ns - T_{setup} + T_{clk1} > D_A \quad (A \rightarrow S1/O)$$

$$10ns - T_{setup} + T_{clk2} > T_{clk1} + 0.5 \quad (S1/clk \rightarrow S2/O)$$

$$10ns - T_{setup} + T_{clk4} > T_{clk1} + 0.5 + (4 + 2 + 3) \quad (S1/clk \rightarrow S4/O)$$

$$(10ns - D_{O2} > T_{clk1} + 0.5 + 4 + 2) \quad (S1/clk \rightarrow O2)$$

$$10ns - T_{setup} + T_{clk3} > T_{clk2} + 0.5 \quad (S2/clk \rightarrow S3/O)$$

$$10ns - T_{setup} + T_{clk4} > T_{clk2} + 0.5 + 4 + 3 \quad (S2/clk \rightarrow S4/O)$$

$$(10ns - D_{O1} > T_{clk3} + 0.5 + 4 + 2) \quad (S3/clk \rightarrow O1)$$

$$(10ns - D_{O1} > T_{clk4} + 0.5 + 2) \quad (S4/clk \rightarrow O1)$$

B2. (3pts) Write the timing inequality for hold time in terms of Tclk1, Tclk2, Tclk3, Tclk4, D_A , D_{O1} , D_{O2} .

$T_{hold} = 0.1$
 $T_{s/p} = 0.5$
 $T_{clk1} = 0.3$
 $T_{clk2} = 0.15$

+3

hold check: $AT > RT$

$D_a > T_{hold} + T_{clk1} \quad (A \rightarrow S_1/b)$

$D_a + 4 + 2 + 3 > T_{hold} + T_{clk4} \quad (A \rightarrow S_4/b)$

$T_{clk1} + 0.5 > T_{hold} + T_{clk2} \quad (S_1/clk \rightarrow S_2/b)$

$T_{clk1} + 0.5 + 4 + 3 > T_{hold} + T_{clk4} \quad (S_1/clk \rightarrow S_4/b)$

$T_{clk2} + 0.5 > T_{hold} + T_{clk3} \quad (S_2/clk \rightarrow S_3/b)$

$T_{clk2} + 0.5 + 4 + 3 > T_{hold} + T_{clk4} \quad (S_2/clk \rightarrow S_4/b)$

B3. (3pts) If T_{setup} (Setup Time) = 0.5ns, T_{hold} (Hold Time) = 0.1ns, $D_A = D_{01} = D_{02} = 0.5ns$, $T_{clk1} = 0.3ns$, $T_{clk2} = 0.15ns$, $T_{clk3} = T_{clk4} = 0ns$.

Explain if there are setup time and hold time violations in this circuit. If yes, identify the violated path(s).

Setup violations:

$S_1/clk \rightarrow S_4/D$ \checkmark $slack = RT - AT = (10 - 0.5 + 0) - (0.3 + 0.5 + 4 + 2 + 3) = -0.3$ \checkmark (violate)
 \uparrow
 critical path


hold violations


$A \rightarrow S_1/D$ $slack = AT - RT = (0.5) - (0.1 + 0.3) = 0.1$ (met) \times
 no

not hold time

bottle neck.

 B4. (4pts) Following part B2, if there are setup/hold time violations in this circuit, how to perform **retiming** to solve these issues (Assume the added registers have the same Tclk as the removed one)? Please draw your circuit and show that no setup and hold time violations exists.



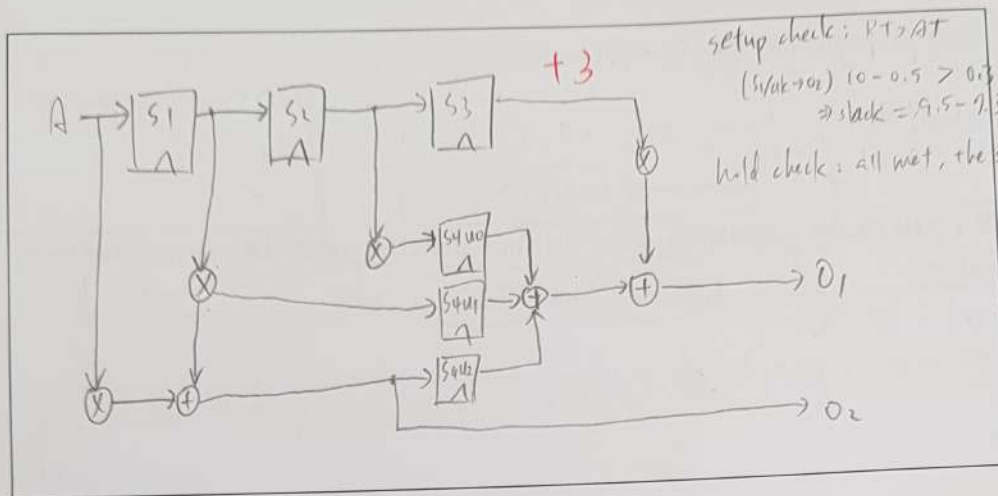


7. (7pts) Slack graph

The following figure shows a combinational circuit with primary inputs A, B, C, and D. Arrival time of these primary inputs are 0.5ns, 1.5ns, 1ns, and 2ns respectively. The delay of each gate is listed below:

XOR	INV	AND3	AND2	OR
4ns	1ns	3ns	2ns	2ns

Assume delay values of wires are zero.

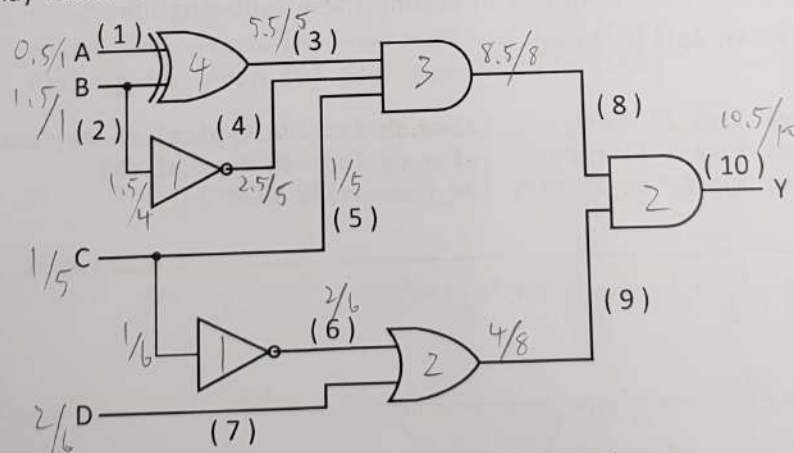

C1. (2%) Write down the arrival time of the output of each edge.

1110 = [0.5, 1.5, 5.5, 2.5, 1, 2, 2, 8.5, 4, 10.5]

C2. (3pts) Given the require time at Y to be 10ns, compute require time and slack

$$RT[1:10] = [1, 1, 5, 5, 5, 6, 6, 8, 8, 10]$$

$$s(a/c)[1:10] = [0.5, -0.5, -0.5, 2.5, 4, 4, 4, -0.5, 4, -0.5]$$

C3. (2pts) Please indicate the critical path and show the critical path by required time values

$$(2) \rightarrow (3) \rightarrow (8) \rightarrow 10$$

$$RT: 1.5 \rightarrow 5.5 \rightarrow 8.5 \rightarrow 10.5$$

8. (35pts) Synthesis

1. Please explain the purposes of setting these following libraries in logic synthesis stage. (4pts, 2pts for each)


- a. `set link_library {slow.db fast.db typical.db dw_foundation.sldb}`
- `set target_library {slow.db fast.db typical.db}`
- b. `set synthetic_library {dw_foundation.sldb }`

a. Specify technology libraries, containing timing/area info for synthesis.

b. Provide timing/area info for designware IPs.

2. What is the problem we may encounter when performing logic synthesis for the following circuit? (3pts)

-2

 


Combinational loop, hard to perform STC.

STA?

3. Please explain the meaning of commands for the corresponding circuit. (2pts)

-1

 

set_false_path -from {A} -through {C} -to {OUT}
set_false_path -from {B} -through {D} -to {OUT}

Don't repeat timing violations for the 2 paths.
analyze

4. Please explain the clock skew and jitter. (4pts, 2pts for each)

skew: the time difference of clk to arrive at different flops.
jitter: the time difference of clk period among cycles.

5. Please explain the following commands for clock setting. (10pts, 2pts for each)

- a. `create_clock -name clk -period 10 clk`
- b. `set_fix_hold` [get_clocks clk]
- c. `set_dont_touch_network` [get_clocks clk]
- d. `set_ideal_network` [get_ports clk]
- e. `set_clock_uncertainty 0.1` [get_clocks clk]

- a. specify clk port and set timing constraint for clk period
- b. fix hold time violations via buffer insertion,
- c. don't optimize clk network since clk tree should not be generated here,
- d. set clk delay to 0
- e. consider clk uncertainty of 0.1 ns since clk arrival time at flops varies,

6. In synthesis stage for low power circuit design, we will use the following command to include both HVT (high-threshold voltage) and RVT (regular-threshold voltage) cells, please explain the advantage for this process. (3pts)

`set_target_library "rvt.db hvt.db"`

For long paths, use RVT to meet timing constraint.
For short paths, use HVT to reduce power consumption.

7. When performing timing analysis with the following command, if there are **only** two paths in the timing report *Design.timing* shown as the following table, please indicate which path is the critical path (1pt) and explain why. (2pts)

```
report_timing -path full -delay max > Design.timing
```

Path1			Path2		
Startpoint: Y[1] (input port clocked by clk) Endpoint: FB_A[10] (output port clocked by clk) Path Group: clk Path Type: max			Startpoint: Y[0] (input port clocked by clk) Endpoint: FB_A[11] (output port clocked by clk) Path Group: clk Path Type: max		
Point	Incr	Path	Point	Incr	Path
clock clk (rise edge)	0.00	0.00	clock clk (rise edge)	0.00	0.00
clock network delay (ideal)	0.50	0.50	clock network delay (ideal)	0.50	0.50
input external delay	5.00	5.50 r	input external delay	5.00	5.50 f
Y[1] (in)	0.00	5.50 r	Y[0] (in)	0.00	5.50 f
U620/Y (CLKINX1)	0.04	5.55 f	U622/Y (CLKINX1)	0.04	5.54 r
U619/Y (MXI2X1)	0.12	5.66 r	U621/Y (MXI2X1)	0.09	5.63 f
U293/CO (ADDFXL)	0.61	6.27 r	U432/Y (AND2X1)	0.21	5.84 f
U294/CO (ADDFXL)	0.33	6.60 r	U432/Y (AND2X1)	0.36	6.19 f
U430/Y (AND2X1)	0.19	6.79 r	U293/CO (ADDFXL)	0.39	6.58 f
U429/Y (XOR2X1)	0.16	6.95 f	U294/CO (ADDFXL)	0.21	6.79 f
U702/Y (MXI2X1)	0.56	7.51 r	U430/Y (AND2X1)	0.18	6.97 f
U363/Y (INVX12)	0.75	8.26 f	U428/Y (AND2X1)	0.15	7.12 f
FB_A[10] (out)	0.00	8.26 f	U427/Y (XOR2X1)	0.54	7.66 r
data arrival time		8.26	U701/Y (MXI2X1)	0.74	8.41 f
			U368/Y (INVX12)	0.00	8.41 f
clock clk (rise edge)	10.00	10.00	FB_A[11] (out)		8.41
clock network delay (ideal)	0.50	10.50	data arrival time		8.41
clock uncertainty	-0.10	10.40			
output external delay	-0.50	9.90	clock clk (rise edge)	10.00	10.00
data required time		9.90	clock network delay (ideal)	0.50	10.50
			clock uncertainty	-0.10	10.40
data required time		9.90	output external delay	-0.50	9.90
data arrival time		-8.26	data required time		9.90
slack (MET)		1.64	data required time		9.90
			data arrival time		-8.41
			slack (MET)		1.49

Path 2.

lower slack.

8. Please explain the reason why we should add the following code in initial block in the test bench for gate level simulation. (3pts)

```
$sdf_annotate(sdf_file.sdf, test_bench_module.top_instance);
```

Sdf files contain timing info. of the cells in netlist, without which the timing check in simulation will not be accurate.

9. Why the synthesis report shows register with latch type when loading design? (1pt) and please also explain how to avoid this situation. (2pts)

Register Name	Type	Width	Bus	MB	AR	AS	SR	SS	ST
reg_B_reg	Latch	8	Y	N	Y	N	N	N	N
reg_ins_reg	Flip-flop	4	Y	N	Y	N	N	N	N
alu_out_reg	Flip-flop	8	Y	N	Y	N	N	N	N
reg_A_reg	Flip-flop	8	Y	N	Y	N	N	N	N

Combinational loop is found

Avoid partially specified condition coding style.
eg. if without else, case without default