

1. Code Debugging and Simulation (10pts)

A. (6pts) Identify syntax and semantic errors. Correct them and put annotations.
Miss one error or mistake one error will minus 1 point until 0.

```
module value_multiplier (
    clk, // Clock
    rst_n, // Asynchronous reset active low
    valueA,
    valueB,
    valueSum
```

No comma after last input/output
Add ; at the end

```
input clk;
input rst_n;
input [3:0] valueA;
input [3:0] valueB;
output [7:0] valueSum;
```

```
reg [3:0] valueA_r, valueB_r;
```

```
reg [7:0] valueSum_r;
```

```
reg [7:0] valueA_sgnExt, valueB_sgnExt;
```

```
reg [7:0] multiply_result;
```

use "assign" should use "wire"

```
assign valueA_sgnExt = {4{valueA_r[3]}, valueA_r};
```

```
assign valueB_sgnExt = {4{valueB_r[3]}, valueB_r};
```

```
assign multiply_result = valueA_sgnExt * valueB_sgnExt;
```

```
assign valueSum = valueSum_r;
```


```

always (posedge clk or negedge rst_n) begin
    if (rst_n) begin
        valueA_r <= 0;
        valueB_r <= 0;
        valueSum_r <= 0;
    end else begin
        valueA_r <= valueA;
        valueB_r <= valueB;
        valueSum_r <= multiply_result;
    end
end
endmodule

```

Handwritten notes:
 - Above the first line: $n/4 \times 8$
 - Next to `posedge clk`: $\neq \text{active low}$
 - Next to `negedge rst_n`: \checkmark
 - Next to `end`: \checkmark
 - Next to `endmodule`: \checkmark
 - Below the code: \hookrightarrow 少个 always block 的 end

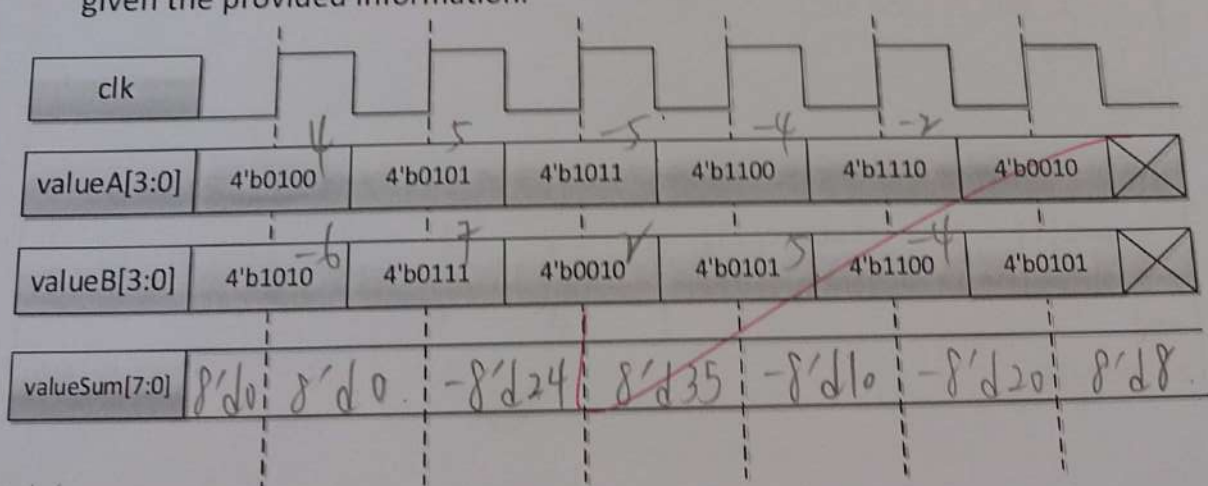B. (4pts) Please show the waveform for the circuit in part A. Suppose that the signal **valueSum** is reset to zero in the beginning and all the syntax error and functionality are correct. Use "xx" to indicate values that cannot be determined given the provided information.



2. Finite State Machine and Simulation (8pts)

Given a Finite-State-Machine (FSM) as below.

```
module FSM (clk, rst_n, in, out_r);
    parameter S0 = 2'b00, S1 = 2'b01, S2 = 2'b10, S3 = 2'b11;

    input clk, rst_n, in;
    output [1:0] out_r;

    reg [1:0] out_r, out;
    reg [1:0] state_c, state_n;

    always @(*) begin
        case(state_c)
            S0: state_n = (in == 1'b0) ? S2 : S0;
            S1: state_n = (in == 1'b0) ? S0 : S3;
            S2: state_n = (in == 1'b1) ? S1 : S3;
            S3: state_n = (in == 1'b1) ? S2 : S1;
        endcase
    end



    always @(posedge clk or negedge rst_n) begin
        if(~rst_n) begin
            state_c <= S0;
            out_r <= 2'b00;
        end
        else begin
            state_c <= state_n;
            out_r <= out;
        end
    end

    always @(*) begin
        out[1] = in ^ state_c[1];
        out[0] = in & state_c[0];
    end
endmodule
```

	S ₁	S ₂	
0	1	1	
1	0	1	

(a) (3pts) Please draw a Mealy state transition graph below for this FSM.

Example

  

- (b) (5pts) The FSM is included as a design under test (DUT) in the testbench. After simulation, the terminal shows the outputs. Please design a DUT and input pattern to test all the possible paths (include self-loops) based on operations of the FSM within the given period.
(You should only change the value of in on negedge clk)

```
module testbench;
reg clk, rst_n, in;
wire [1:0] out_r;
FSM DUT(.clk(clk), .rst_n(rst_n), .in(in), .out_r(out_r));
always @(*) begin
    $monitor("%t clk=%b rst_n=%b in=%b state_c=%d out_r=%b",
        $time, clk, rst_n, in, DUT.state_c, out_r);end
// ...
endmodule
```

Monitor Output Response:

Time	clk	rst_n	in	state_c	out_r
0	1	0	1	S0	00
1	0	1	1	S0	00
2	1	1	1	S0	10
3	0	1	0	S0	10
4	1	1	0	S2	00
5	0	1	0	S2	00
6	1	1	0	S3	10
7	0	1	0	S3	10
8	1	1	0	S1	10
9	0	1	1	S1	10
10	1	1	1	S3	11
11	0	1	1	S3	11
12	1	1	1	S2	01
13	0	1	1	S2	01
14	1	1	1	S1	00
15	0	1	0	S1	00
16	1	1	0	S0	00


3. Logic Synthesis + Blocking & Non-Blocking (12 pts)

Please draw the corresponding circuits (in the right column) according to the Verilog codes (in the left column). You can use AND, OR, NAND, NOR, XOR, XNOR, NOT, MUX, D Flip-Flop, Latch, Shifter, Adder, Multiplier in the circuit diagram.

(a) Verilog Code (3 pts)	Circuit Diagram
<pre> always @(*) begin X = A + B << 2; Z = C D; Y = (~Z) ? X : Q; end </pre>	
(b) Verilog Code (3 pts)	Circuit Diagram
<pre> always @(posedge clk) begin A <= D; B <= A ~^ D; C <= ~B; D <= C ^ D; end </pre>	
(c) Verilog Code (3pts)	Circuit Diagram
<pre> always @(A or B or C) begin if (~C) D = A & B; end </pre>	
(d) Verilog Code (3pts)	Circuit Diagram
<pre> always @(posedge clk) begin if (C) D <= A ~B; end </pre>	

 4. Verilog Design (6pts)

A design with an ALU unit and its description of functions are shown below.



Signal	Description
clk	Input clock
rst_n	Input asynchronous negative reset
data_in [7:0]	Input unsigned data
accum [7:0]	Result from ALU
data_out [7:0]	Output unsigned data (positive clock edge triggered)
opcode [1:0]	Input operation control signals

opcode	ALU operation
2'b00	A + B
2'b01	A - B
2'b10	A XOR B
2'b11	A NOR B

(6pts) Please complete the Verilog code of this counter (you don't have to consider overflow in this design).

```
module alu_design (clk, rst_n, opcode, data_in, data_out);
```

I/O & Reg/Wire Declaration (1pt)

```
input clk, rst_n;
input [1:0] opcode;
input [7:0] data_in;
output [7:0] data_out;
```

// You can declare new signals here if you need

```
reg [7:0] accum;
reg [7:0] data_out;
```


Combinational Logic for the Counter (3pts)

always @ (*) begin

case(opcode)

2'b00: accum = data_in + data_out;

2'b01: accum = data_in - data_out;

2'b10: accum = data_in ^ data_out;

2'b11: accum = ~(data_in | data_out);

endcase

end

Sequential Logic for the Counter (2pts)

always @ (posedge clk or negedge rst_n) begin

if (!rst_n) begin

data_out <= 8'b0;

end else begin

data_out <= accum;

end.

end

endmodule


5. Formal Verification (9pts)

Consider 3 assertions and 4 patterns below. Please identify the patterns which are violated for each assertion.

(a) assert_0: assert property (@(posedge clk)
 $\neg(\text{GntB} \ \&\& \ !\text{Busy})$)

(b) assert_1: assert property (@(posedge clk)
 $\text{GntA} \ \&\& \ !\text{GntB} \ \rightarrow \ \#\#[0:2] \ \text{Busy}$)

(c) assert_2: assert property (@(posedge clk)
 $\text{GntA} \ || \ \text{GntB} \ \rightarrow \ \text{Busy}$)

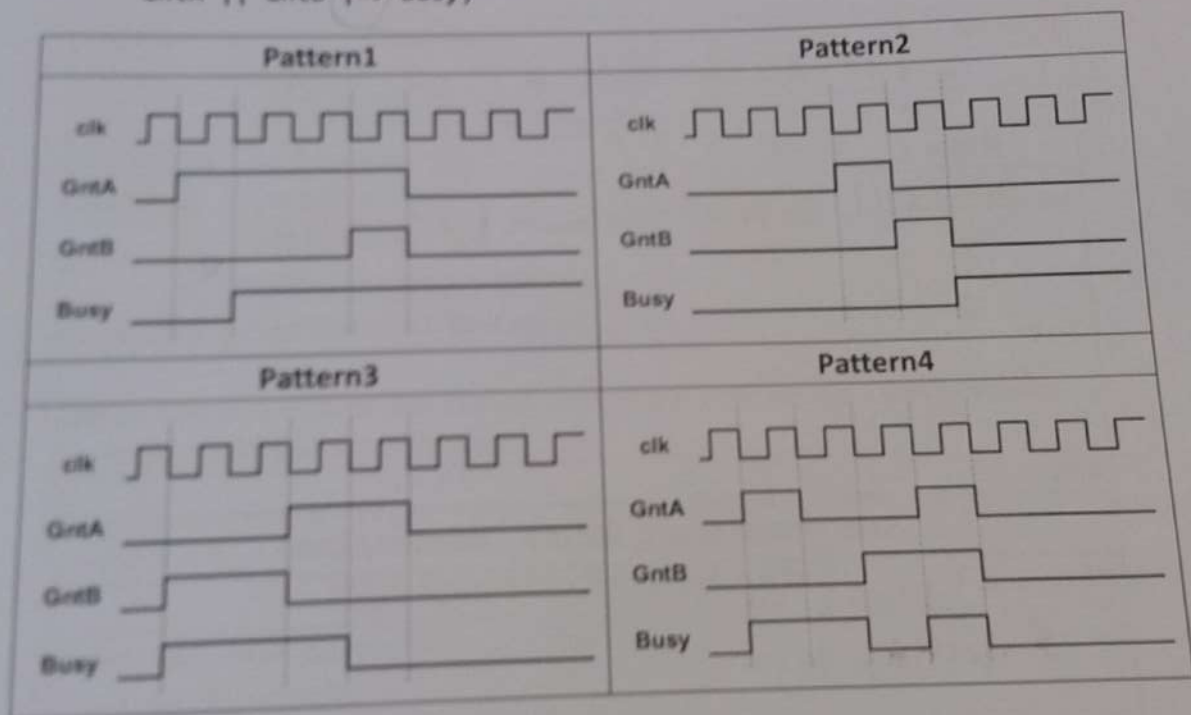


(9 pts) Fill in Pass/Fail in each block.

	Pattern1	Pattern2	Pattern3	Pattern4
(a)	Pass	Fail	Pass	Fail
(b)	Pass	Pass	Fail	Pass
(c)	Pass	Fail	Fail	Fail

10/21

 6. Timing path & Setup/hold time (22pts)

Consider the circuit and the delay information below. Answer the following questions.




Operation	\oplus	\otimes	$ \cdot $	x^2
Min Delay (ns)	0.5	3.0	0.2	1.5
Max Delay (ns)	1.0	4.0	0.5	2.0

A. (5pts) List all timing paths. How many timing paths in total? (e.g. A \rightarrow S1/D)

A \rightarrow S2/D
 S2/clk \rightarrow C
 S2/clk \rightarrow S2/D
 B \rightarrow S1/D
 S1/clk \rightarrow S2/D
 S1/clk \rightarrow S3/D
 S3/clk \rightarrow S3/D
 S3/clk \rightarrow S2/D

8 paths

B. Setup/Hold time constraint

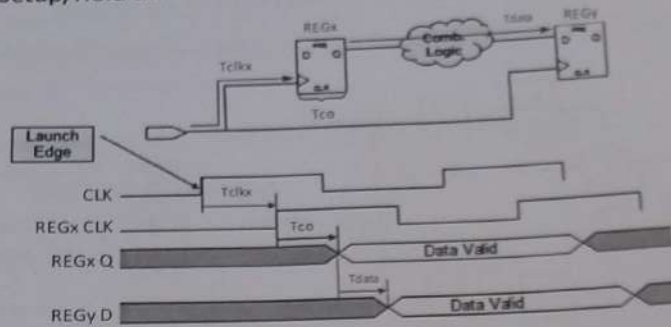

Following the circuit in 6.A. The registers' timing diagrams are shown above. $T_{co} = 0.5\text{ns}$, and $T_{clk} = 0.3\text{ns}$ are the same for every register. Assuming that T_{setup} (Setup Time) = 0.4ns , T_{hold} (Hold Time) = 0.1ns , and $D_A = D_B = D_C = 1.5\text{ns}$. The circuit operates at the clock frequency of 125MHz . 8ns

B1. (5pts) Check that whether there are setup time violations or not by showing if the related inequalities for all timing paths are satisfied. If setup time violation(s) occur, identify the violated path(s).

$$RT > AT \quad (\text{cycle time} + T_{clk} - T_{setup} > T_{clk} + T_{co} + T_{pd})$$

(Met) $A \rightarrow S^2/D : 8 + 0.3 - 0.4 > 1.5 + 4$ ✓

(Met) $B \rightarrow S^1/D : 8 + 0.3 - 0.4 > 1.5$ ✓

(Met) $S^2/clk \rightarrow C : 8 - 1.5 > 0.3 + 0.5 + 2$ ✓

(Met) $S^2/clk \rightarrow S^2/D : 8 + 0.3 - 0.4 > 0.3 + 0.5 + 2 + 1 + 4$ ✓

(Met) $S^1/clk \rightarrow S^2/D : 8 + 0.3 - 0.4 > 0.3 + 0.5 + 1 + 1 + 4$ ✓

(Met) $S^1/clk \rightarrow S^3/D : 8 + 0.3 - 0.4 > 0.3 + 0.5 + 1$ ✓

(Met) $S^3/clk \rightarrow S^3/D : 8 + 0.3 - 0.4 > 0.3 + 0.5 + 0.5 + 1$ ✓

(Met) $S^3/clk \rightarrow S^2/D : 8 + 0.3 - 0.4 > 0.3 + 0.5 + 0.5 + 1 + 1 + 4$ ✓

No setup-time violation

B2. (5pts) Check that whether there are hold time violations or not by showing if the related inequalities for all timing paths are satisfied. If hold time violation(s) occur, identify the violated path(s).

$$RT < AT \quad (T_{clk} + T_{hold} < T_{clk} + T_{co} + T_{cd})$$

(Met) $A \rightarrow S_2/B : 0.3 + 0.1 < 1.5 + 3$ ✓

(Met) $B \rightarrow S_1/B : 0.3 + 0.1 < 1.5$ ✓

(Met) $S_2/clk \rightarrow C : -1.5 < 0.3 + 0.5 + 1.5$ ✓

(Met) $S_2/clk \rightarrow S_2/B : 0.3 + 0.1 < 0.3 + 0.5 + 1.5 + 0.5 + 3$ ✓

(Met) $S_1/clk \rightarrow S_2/B : 0.3 + 0.1 < 0.3 + 0.5 + 0.5 + 0.5 + 3$ ✓

(Met) $S_1/clk \rightarrow S_3/B : 0.3 + 0.1 < 0.3 + 0.5 + 0.5$ ✓

(Met) $S_3/clk \rightarrow S_3/B : 0.3 + 0.1 < 0.3 + 0.5 + 0.2 + 0.5$ ✓

(Met) $S_3/clk \rightarrow S_2/B : 0.3 + 0.1 < 0.3 + 0.5 + 0.2 + 0.5 + 0.5 + 3$ ✓

⇒ No hold time violation

B3. (7pts) Assuming that there is time skew between T_{clk3} and other T_{clk} , the relationship between those parameters is: $T_{clk3} = T_{clki} + 0.1 * Clk_cycle$, where $i = 1, 2$. T_{clk1} , T_{clk2} , and other conditions are the same as A2. Explain if there are timing violations in this circuit. If yes, identify the violated path(s).

$$T_{clk1}, T_{clk2} = 1.1$$

Setup time:

(Met) $S_1/clk \rightarrow S_3/B : 8 + 1.1 - 0.4 > 0.3 + 0.5 + 1$ ✓

(Met) $S_3/clk \rightarrow S_3/B : 8 + 1.1 - 0.4 > 1.1 + 0.5 + 0.5 + 1$ ✓

(Violated) $S_3/clk \rightarrow S_2/B : 8 + 0.3 - 0.4 > 1.1 + 0.5 + 0.5 + 1 + 1 + 4 \Rightarrow 7.9 > 8$ (X)
 $\Rightarrow S_3/clk \rightarrow S_2/B$ has setup time violation

hold time:

(Met) $S_1/clk \rightarrow S_3/B : 1.1 + 0.1 < 0.3 + 0.5 + 0.5$ ✓


(Met) $S_3/clk \rightarrow S_3/B : 1.1 + 0.1 < 1.1 + 0.5 + 0.2 + 0.5$ ✓

(Met) $S_3/clk \rightarrow S_2/B : 0.3 + 0.1 < 1.1 + 0.5 + 0.2 + 0.5 + 0.5 + 3/21$ ✓

No hold time violation

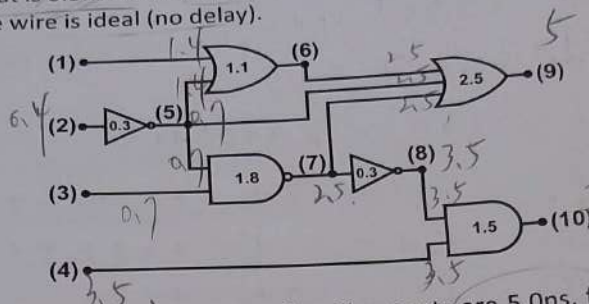7. Slack graph (8pts)

The figure below shows a combinational circuit with primary inputs. The delay of each input is 0.3ns and the delay of every gate is given on the gate (unit: ns). Assume the wire is ideal (no delay).



C1. (5pts) Given the required time for all outputs are 5.0ns, fill the blanks on the form with corresponding arrival time, required time, and slack of every node.
AT = Arrival Time, RT = Required Time.


Node	(1)	(2)	(3)	(4)	(5)
AT (ns)	0.3	0.3	0.3	0.3	0.6
RT (ns)	1.4	0.4	0.7	3.5	0.7
Slack (ns)	1.1	0.1	0.4	3.2	0.1
Node	(6)	(7)	(8)	(9)	(10)
AT (ns)	1.7	2.4	2.7	4.9	4.2
RT (ns)	2.5	2.5	3.5	5.0	5.0
Slack (ns)	0.8	0.1	0.8	0.1	0.8

C2. (3pts) Please indicate the critical path and show its slack values.

$(2) \rightarrow (5) \rightarrow (7) \rightarrow (9) = \text{slack} = 0.1 \text{ at all nodes.}$

 
8. Synthesis (33pts)

- Please explain why synthesis is constraint-driven and what is the meaning of the tradeoff between area and speed according to the following image. (2pts)




① Constraint-driven 代表由 designer 決定希望得到較好 area/timing 或 power 的 performance 而在 sdc 或 tel 檔中下相對應的指令 (constraint) 合成時是依據這些 constraint 來針對 area/power/timing 進行優化。② 若希望 timing fast 則 area 勢必有所犧牲而變大

 - Why we preferred the architecture on the right hand side instead of left hand side design in clock gating? (2pt)



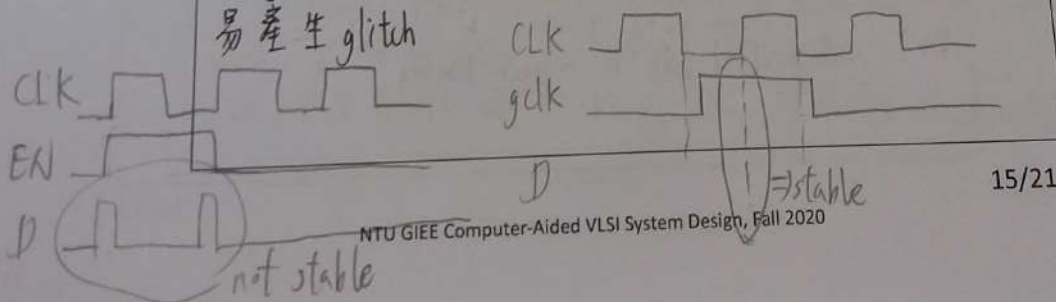
為了讓 EN 使用 falling edge trigger 的 cycle 易產生 glitch



3. Please explain why should we consider PVT condition when synthesis (1pt) and what does PVT stand for? (1pt)

PVT 代表 operating condition, 根據製程. 電壓. 溫度不同而造成 gate/cell 的 timing delay / area 有所差異
P: process 製程 (越小越 fast) 而能定義出
V: voltage 電壓 (越大越 fast) max-delay: check setup time
T: temperature 溫度 (越低越 fast) min-delay: check hold time

 4. What is the problem we may encounter when performing logic synthesis for the following circuit? (1pt) and how to avoid this situation? (1pt)



Combinational-loop may cause STA to have race-condition
⇒ 無法做 timing analysis
To avoid: Break the combinational loop here


5. In synthesis stage for low power circuit design, we will use the following command to include both HVT (high-threshold voltage) and RVT (regular-threshold voltage) cells, please explain the advantage for this process. (2pts)

`set_target_library "rvt.db hvt.db"`

HVT: let non-critical path to save power

RVT: let critical path to improve timing

 6. In a hierarchical design, submodules are sometimes referenced by more than one cell instance. What method is required to solve this situation? (1pt)
And what is the effect after applying this method? (1pt)



uniquify = 將 reference 到同一個 submodule 的 cell instance 分開, 當作是不同的 submodule 處理
能對於 timing、area 各自進行優化得到更好結果 (performance)
~~但會執行~~ 且能保留其 hierarchy

7. Please explain the difference between RTL Level Netlist and Gate Level Netlist. (1pt)

RTL 使用 assign、always block 描述電路
gate-level 使用 AND、OR 等邏輯閘描述電路。
RTL 經 synthesis 後可得 gate-level netlist 及 FF 等

8. Please explain why we should add the following code into the testbench when performing gate level simulation. (1pt)

```
$sdf_annotate ("SDF_FILE_NAME", top_module_instance_name);
```

否則執行 gate-level simulation 時會使用 cell_model (tsmc13...) default 的 timing delay 而導致錯誤
sdf 裡定義 cell/gate 的 timing delay 用來做 simulation 才正確

9. Why the synthesis report shows register with latch type when loading design? (1pt) and please also explain how to avoid this situation. (1pt)

Register Name	Type	Width	Bus	MB	AR	AS	SR	SS	ST
reg_B_reg	Latch	8	Y	N	Y	N	N	N	N
reg_ins_reg	Flip-flop	4	Y	N	Y	N	N	N	N
alu_out_reg	Flip-flop	8	Y	N	Y	N	N	N	N
reg_A_reg	Flip-flop	8	Y	N	Y	N	N	N	N

在 combinational part 中的 reg-B 的 next state 值沒有在所有情況下皆 assign 值，例如 if-else 或 case 中某些 branch 未定義該值，或未使用 default branch
 solution: 在 combinational part - 開始就給予 default 值，例如: reg-B-w = reg-B-r;
 或是所有 if-else branch 及 case 中給予 default 值，且寫滿所有 branch

10. Synopsys Design Constraints File (.sdc) specifies the timing constraints for synthesis. Please write the commands might be included in the .sdc file to meet the following specification. (10pts, 1pt for each)

- A. This design is an ALU with clock port i_clk with 200 MHz operating frequency (1%)
 B. All flip-flops should meet the hold-time constraints (1%)
 C. Clock tree synthesis will be built in the place and route stage, so the clock network cannot be re-buffered (1%)
 D. Clock tree synthesis will be built in the place and route stage, so the clock network is considered with no delay (1%)
 E. The input delay is considered as $0.1 \times \text{clock_cycle}$ (1%)
 F. The output delay is considered as $0.1 \times \text{clock_cycle}$ (1%)
 G. The operating condition for synthesis should include both *slow* and *fast* library for *max* and *min* condition (1%)
 H. The clock latency is considered as $0.05 \times \text{clock_cycle}$ (1%)
 I. The clock transition is considered as $0.01 \times \text{clock_cycle}$ (1%)
 J. The clock skew and jitter are considered as 0.1 ns and 0.2ns, respectively (1%)

These are only example commands you may use, please choose the correct ones and modify them to meet the abovementioned specification. (you do not have to consider the commands for including library)

- set period 10.0
- set_operating_conditions -max_library slow -max slow
- create_clock -name clk -period 10.0

4. set_dont_touch_network [get_clocks clk]
5. set_ideal_network [get_clocks clk]
6. set_fix_hold [get_clocks clk]
7. set_clock_latency 0.5 [get_clocks clk]
8. set_clock_transition 0.1 [get_clocks clk]
9. set_max_transition 0.1
10. set_input_delay 0.5 -clock clk [all_inputs]
11. set_output_delay 0.5 -clock clk [all_outputs]
12. set_clock_uncertainty 0.1 [get_ports clk]
13. set_load 1 [all_outputs]
14. set_drive 1 [all_inputs]
15. set_false_path -from {A} -through {C} -to {OUT}
16. set_max_delay 1 from [all_inputs] -to [all_outputs]

- A. create_clock -name i-clk -period 5.0
- B. set_fix_hold [get_clocks i-clk]
- C. set_dont_touch_network [get_clocks i-clk]
- D. set_ideal_network [get_clocks i-clk]
- E. set_input_delay 0.5 -clock i-clk [all_inputs]
- F. set_output_delay 0.5 -clock i-clk [all_outputs]
- G. set_operating_conditions -max_library slow -max_slow -min_library fast -min_fast
- H. set_clock_latency 0.5 [get_clocks i-clk]
- I. set_clock_transition 0.05 [get_clocks i-clk]
- J. set_clock_uncertainty 0.3 [get_clocks i-clk]

11. Two situations are considered for clock uncertainty: clock skew and clock jitter. Please explain the definition of clock skew (1pt) and clock jitter (1pt).

skew: (On-chip) spatial variation of the arrival time of clock
(不同 FF 間 clock 的 arrival time 可能有差異)

jitter: (Off-Chip) temporal variation of a clock-period in the same
Flip-Flop (同-FF 的 cycle time 可能有差異)

19/21

12. Please read the area synthesis report below and answer the related questions:

- How to fix the undefined interconnect area? (1pt)
- If Macro/Black Box area is not zero, what might be indicated? (1pt)
- In cell-based IC design flow, we will mainly focus on total cell area instead of total area, please explain why. (1pt)

```

1 *****
2 *****
3 Report : area
4 Design : ALU
5 Version: N-2017.09-SP2
6 Date   : Fri Nov 13 12:55:25 2020
7 *****
8
9 Library(s) Used:
10
11   typical (File: /home/raid7_2/course/cvcd/CBCK_IC_Context/CIC/Synopsys/CIC/dh/typical.dh)
12
13 Number of ports:          82
14 Number of nets:          204
15 Number of cells:         106
16 Number of combinational cells:  74
17 Number of sequential cells:    30
18 Number of macros/black boxes:   6
19 Number of buf/inv:             10
20 Number of references:          16
21
22 Combinational area:        977.702419
23 Buf/Inv area:              37.342799
24 Noncombinational area:     903.016769
25 Macro/Black Box area:      0.000000
26 Net Interconnect area:     undefined
27
28 Total cell area:           1880.719188
29 Total area:                undefined

```

a. use "set-wire-load-model" to 估計 net/wire 的 area

b. 有使用 external IP, 例如 SRAM

c. 在合成階段所估計的 net/wire area 相當不準確
因此只先考慮 total cell area

13. When performing timing analysis with the following command, if there are *only* two paths in the timing report *Design.timing* shown as the following table, please indicate which path is the critical path (1pt) and explain why. (1pt)

```
report_timing -path full -delay max > Design.timing
```

Path1			Path2		
Startpoint: V[0] (input port clocked by clk) Endpoint: FB_A[11] (output port clocked by clk) Path Group: clk Path Type: max			Startpoint: V[1] (input port clocked by clk) Endpoint: FB_A[10] (output port clocked by clk) Path Group: clk Path Type: max		
Point	Incr	Path	Point	Incr	Path
clock clk (rise edge)	0.00	0.00	clock clk (rise edge)	0.00	0.00
clock network delay (ideal)	0.50	0.50	clock network delay (ideal)	0.50	0.50
input external delay	5.00	5.50 f	input external delay	5.00	5.50 r
V[0] (in)	0.00	5.50 f	V[1] (in)	0.00	5.50 r
U622/Y (CLKINX1)	0.04	5.54 r	U629/Y (CLKINX1)	0.04	5.55 f
U621/Y (MXI2X1)	0.09	5.63 f	U619/Y (MXI2X1)	0.12	5.66 r
U432/Y (AND2X1)	0.21	5.84 f	U293/CO (ADDFXL)	0.61	6.27 r
U293/CO (ADDFXL)	0.36	6.19 f	U294/CO (ADDFXL)	0.33	6.66 r
U294/CO (ADDFXL)	0.39	6.58 f	U430/Y (AND2X1)	0.19	6.79 r
U430/Y (AND2X1)	0.21	6.79 f	U429/Y (XOR2X1)	0.16	6.95 f
U428/Y (AND2X1)	0.18	6.97 f	U702/Y (MXI2X1)	0.56	7.51 r
U427/Y (XOR2X1)	0.15	7.12 f	U363/Y (INVX12)	0.75	8.26 f
U701/Y (MXI2X1)	0.54	7.66 r	FB_A[10] (out)	0.00	8.26 f
U368/Y (INVX12)	0.74	8.41 f	data arrival time		8.26
FB_A[11] (out)	0.00	8.41 f			
data arrival time		8.41	clock clk (rise edge)	10.00	10.00
			clock network delay (ideal)	0.50	10.50
clock clk (rise edge)	10.00	10.00	clock uncertainty	-0.10	10.40
clock network delay (ideal)	0.50	10.50	output external delay	-0.50	9.90
clock uncertainty	-0.10	10.40	data required time		9.90
output external delay	-0.50	9.90	data required time		9.90
data required time		9.90	data arrival time		-8.26
data arrival time		-8.41			
slack (MET)		1.49	slack (MET)		1.64

Path 1 is critical path

Since $\text{slack} = \text{required time} - \text{arrival time}$

slack 越小代表 timing 越緊 $\Rightarrow 1.49 < 1.64$

\Rightarrow Path 1 is critical path